

IMPORTANT QUESTION

- 1) Explain working principle of NPN Transistor.
- 2) Explain Output Characteristics of CE configuration, Q point and Dc load line.
- 3) Compare the different configuration of transistor (CB, CE, CC)
- 4) How transistor work as a switch ?
- 4) How transistor work as an Amplifier
- 5) What do you mean by Thermal Runaway and stability Factor?
- 7) Why BJT is Bipolar But FET is unipolar?
- 8) Explain the working and characteristics of FET.
- 9) COMPARISON
 - A● BJT vs FET
 - B● FET vs MOSFET
- 10) What do you mean by Transistor Biasing ?

Write the Name of Different transistor Biasing.

11) Explain Potential divider /Voltage divider Biasing.

12) Explain the Construction of Working of Mosfet.

13). Define the following term

A♦ Bias Stabilisation

B♦ Stability Factor

C♦ Compensation Technique

4♦ Pinch Voltage

Explain the construction of UJT and How it work as a relaxation oscillator?

Digital

1) Conversion from one another
like: \Rightarrow Hexadecimal to another
Any No. System to Decimal

2) Application of Universal Gate

A) NAND

B) NOR

3) Solⁿ of K-Map: \Rightarrow

4) Design the different Combinational Circuits

A) Half Adder

B) Full Adder

C) Encoder

D) Decoder

E) MUX

F) DMUX

5) What do you mean by Flip Flop?

Explain SR Flip flop.

Explain Master-Slave Flip flop.

6) What is Race around condition?
How it is removed?

7) Explain BCD Counter?

8) Write difference between Combinational CKT, Sequential CKT.

9) What do you mean Register? Explain ~~different~~ different types of Register.

10) Explain R-2R ladder Type converter

11) Explain different type of ADC \Rightarrow

A) Counter Type ADC

B) Dual Slope Converter

C) Flash Type Converter / Parallel Converter.